

ISBN: 9788183710787

Electric Circuit Analysis

Second Edition

Dr. P. Ramesh Babu,

Professor and Head,

Department of Electronics and Instrumentation Engineering,

Pondicherry Engineering College,

Pudhucherry - 605 014.



Publishing for future

SCITECH PUBLICATIONS (INDIA) PVT. LTD.

www.scitechpublications.com

www.scitechpublications.com

Copyright © 2006 Scitech Publications (India) Pvt. Ltd.

SCITECH PUBLICATIONS (INDIA) PVT. LTD.

Old No: 3, New No: 5,

Bakthavachalam Street,

Tambaram West, Chennai - 600 045.

E-mail: scitechcorp@yahoo.co.in

Visit us at www.scitechpublications.com

Branches:

Hyderabad: scitech_hyd@yahoo.co.in

Kolkata: scitech_kol@yahoo.co.in

New Delhi: scitech_del@yahoo.co.in

This book or any part thereof may not be reproduced in any form without the written permission of the publisher.

Publisher's Disclaimer

The Publisher of this book declare that the Author of this book has taken the full responsibility for the content of this book, any dispute and copyright violation arising based on the content of this book will be addressed by the author. Furthermore, the author agree to indemnify the publisher from damages arising from such disputes and copyright violation as stated above.

978 81 8371 078 7

Published by M. R. Purushothaman for Scitech Publications (India) Pvt. Ltd., Old No: 3, New No: 5, Bakthavachalam Street, Tambaram West, Chennai - 600 045.

Contents

Chapter 1	Basic Circuit Analysis	1.1 - 1.78
	<ul style="list-style-type: none">• Introduction• Current Direction• Direct Current (DC) and Alternating Current (AC)• Voltage and Energy• Power• Active and Passive Elements• Independent Voltage Source• Independent Current Source• Series Connected Independent Sources• Parallel Connected Independent Sources• Dependent Sources• Resistance and Conductance• Ohm's Law• Networks and Circuits• Kirchoff's Laws<ul style="list-style-type: none">- Kirchoff's Current Law (KCL)- Kirchoff;s Voltage Law (KVL)• Single Loop Circuit<ul style="list-style-type: none">- Resistor in series• Single Node-pair Circuit<ul style="list-style-type: none">- Resistors in parallel• Current Divider• Conductances in Parallel• Series - Parallel Circuits• Analysis of a Ladder Network<ul style="list-style-type: none">- Analysis of R-2R ladder networkl• Equivalent Resistance• Source Transformation• Energy Storage Elements<ul style="list-style-type: none">- Capacitor- Inductor• Response of energy Storage Elements to DC Sources• Short Question and Answers	
Chapter 2	Basic Circuit Analysis	2.1 - 2.36
	<ul style="list-style-type: none">• Introduction• Nodal Analysis<ul style="list-style-type: none">- Circuits containing voltage sources (supernode)	

- Mesh Analysis
 - Supermesh
- Short Question and Answers

Chapter 3 Network Theorems 3.1 - 3.52

- Introduction
- Linearity, Proportionality and Superposition
- Reciprocity Theorem
- Thevenin's Theorem
- Norton's Theorem
- Maximum Power Transfer Theorem
- Delta - Wye Transformations
- Compensation Theorem
- Millmann's Theorem
- Short Question and Answers
-

Chapter 4 Sinusoidal Steady State Analysis 4.1 - 4.66

- Introduction
- Characteristics of Sinusoids
 - Generation of alternating emf
 - Periodicity nature of sinewave
 - Important terms and definitions
 - Phase
 - Phase difference
 - In phase
 - Out of phase
 - Lagging and leading
- Forced Response to Sinusoidal Functions
- Phasor Representation
- The Complex Forcing Function
- Complex Algebra
 - Polar form
 - Arithmetic operations
- Complex Plane
- The operator j
- Phasor Relationship for R, L and C
 - Resistor
 - Inductor
 - Capacitor
- Impedance
- Impedance Diagram

- Admittance
- Phasor Diagram
 - RL series circuit
 - RC series circuit
 - RLC series circuit
- Impedance in Series
- Impedance in Parallel
- AC Circuit Analysis
- Instantaneous Power
- Average Power
- RMS Value of Current and Voltage
- Apparent Power (Complex Power) and Power Factor
- Power Triangle
- Short Question and Answers

Chapter 5 Application of Network Theorems to AC Circuits 5.1 - 5.46

- Introduction
- Mesh and Node Analysis
 - AC mesh analysis
 - AC node analysis
- Delta-Wye Transformations
- Source Transformations
- Superpositions Theorem
- Reciprocity Theorem
- Thevenin's Theorem
- Norton's Theorem
- Compensation Theorem
- Maximum Power Transfer Theorem
- Millman's Theorem
- Short Question and Answers

Chapter 6 Resonance 6.1 - 6.24

- Resonance
- Impedance resonance
- Current at Resonance
- Variation of Capacitor Voltage and Inductor Voltage with Frequency
- Q-Factor
- Band Width
- Parallel Resonance
- Short Question and Answers

Chapter 7 Coupled Circuits 7.1 - 7.30

- Introduction
- Dot Convection
- Coupling Coefficient K
- Transformer
- Short Question and Answers

Chapter 8 Three Phase Systems 8.1 - 8.26

- Introduction
- Three Phase System
- Balanced Loads
 - Balanced wye load
 - Balanced delta load
- Unbalanced Loads
 - Unbalanced delta connected load
 - Unbalanced star connected load
 - Unbalanced three - wire star connected
- Power in Three Phase Balanced Loads
- Two Wattmeter Method of Measurement of Power
- Symmetrical Components
- The 'a' operator
 - Absence of zero sequence components
 - Negative sequence and zero-sequence sources
 - Study of symmetric components using matrices
- Short Question and Answers

Chapter 9 Network Topology 9.1 - 9.22

- Introduction
- Incidence Matrix
- Fundamental Loop Matrix
- Cutset
- Fundamental Cutset and Cutset Matrix
- f-Cutset Matrix
- Tie-set Matrix
- Tie-set Schedule
- Cutset Schedule
- Duality
- Short Question and Answers

Chapter 10 Natural and Forced Response of
RL, RC and RLC Circuits 10.1 - 10.84

- Introduction
- Initial Conditions
- Initial Condition in Circuit Elements
 - Resistor
 - Inductor
 - Capacitor
- Solution of Differential Equations
 - Solution of differential equations (classical methods)
- Basic RL and RC Circuits without Source
 - RL circuit without source
 - RC circuit without source
 - General RL circuit without source
 - General RC circuit without source
- Step Response of RL Circuit
- Step Response of RC Circuit
- RLC Circuit
 - Source free RLC series circuit
 - Parallel RLC circuit
- Short Question and Answers

Chapter 11 The Laplace Transform 11.1 - 11.62

- Introduction
- Laplace Transform
- Laplace Transform of Signal Waveforms
 - Unit step function
 - The shifted unit step function
 - Unit ramp function
 - Shifted ramp function
 - Unit impulse function
 - The exponential function
- Properties of Laplace Transform
 - Linearity
 - Transform of derivatives
 - Transform of the integrals
 - Scaling property
 - Time shift
 - Frequency shift
 - Differentiation in the s-domain
 - Time convolution

- Frequency convolution
- Initial value theorem
- Final value theorem
- Inversion of Laplace Transform
- Distinct poles
- Multiple poles
- Complex roots
- Solving Integrodifferential Equations
- Transient Analysis using Laplace Transforms
- Short Question and Answers

Chapter 12 Network Functions and s-domain Analysis 12.1 - 12.68

- Introduction
- Transform Impedance Elements
 - Resistors in s-domain
 - Inductor in s-domain
 - Capacitor in s-domain
- Nodal and Mesh Analysis in s-domain
- Network Functions for Two-port Network
- Poles and Zeros of Network Functions
- Transfer Function
- Convolution Integral
- Stability
- Stability in s-domain
- Routh-Hurwitz Stability Criterion
- Short Question and Answers

Chapter 13 Two-Port Networks 13.1 - 13.62

- Introduction
- Z-Parameters
- Reciprocal Networks
- Y-Parameters
- Hybrid Parameters
- Transmission Parameters
- Inverse Transmission Parameters
- Relationships between Parameter Sets
 - Y-parameters in terms of Z-parameters
 - Z-parameters in terms of Y-parameters
 - Z-parameters in terms of h-parameters
 - h-parameters in terms of Z-parameters

- Y-parameters in terms of h-parameters
- h-parameters in terms of Y-parameters
- Z-parameters in terms of ABCD parameters
- ABCD parameters in terms of Z-parameters
- ABCD parameters in terms of h-parameters
- h-parameters in terms of ABCD parameters
- Transmission Parameters for Reciprocal Networks
- Two-port Parameters in s-domain
- Cascade Connection of Two-ports
- Parallel Connection of Two Two-port Networks
- Series Connection of Two-port Networks
- Series-Parallel Connection of Two Two-port Networks
- Two-port Network with Terminated Impedance
- Short Question and Answers

Chapter 14 Fourier Series Analysis of Circuits 14.1 - 14.46

- Introduction
- Periodic Waveforms
- Fourier Series
- Evaluation of Fourier Coefficients
- Even and Odd Symmetry
 - Half wave symmetry
- Cosine Representation
- Exponential Fourier Series
- Existence of Fourier Series
- Properties of Continuous-Time Fourier Series
 - Linearity
 - Time shifting
 - Time reversal
 - Time scaling
 - Multiplication
 - Conjugation
 - Parseval's theorem
- Power Representation using the Fourier Series
- Fourier Spectrum
- Network Analysis using Fourier Series
- The Fourier Transform
- Existence of Fourier Transform
- Properties of Fourier Transform
- Circuit Analysis with Fourier Transform
- Short Question and Answers

Chapter 15	Filters	15.1 - 15.58
	<ul style="list-style-type: none">• Introduction• Frequency Selection Filters• Lowpass Filters<ul style="list-style-type: none">- The series RL circuit- A series RC circuit• Highpass Filter• Bandpass Filters• Bandreject Filters• Second Order Lowpass Filter• Second Order Highpass Filter• Analog Lowpass Filter Design<ul style="list-style-type: none">- Analog lowpass Butterworth filter- Analog lowpass Chebyshev filter• Frequency Transformation in Analog Domain<ul style="list-style-type: none">- Lowpass to lowpass- Lowpass to highpass- Lowpass to bandpass- Lowpass to bandstop• Active Filters<ul style="list-style-type: none">- Operational amplifier- The ideal op-amp- Virtual ground- Inverting amplifier- Non-inverting amplifier- First order lowpass filter- First order highpass filter- Second order active filter- Bandpass filter• Short Question and Answers	
Chapter 16	State-Variable Analysis	16.1 - 16.12
	<ul style="list-style-type: none">• Introduction• State Variable• Short Question and Answers	
Chapter 17	Network Synthesis	17.1 - 17.29
	<ul style="list-style-type: none">• Introduction• Hurwitz Polynorminal• Positive Real Functions• Synthesis of Driving Point immittances	

- Foster form I
- Foster form II
- Cauer form I
- Cauer form II
- Short Question and Answers

Appendix A	Solution to Problems Appeared in GATE and IES Examinations	1 - 35
Appendix B	Average and RMS Values	36 - 42
Appendix C	Matrices	43 - 46
Bibliography		