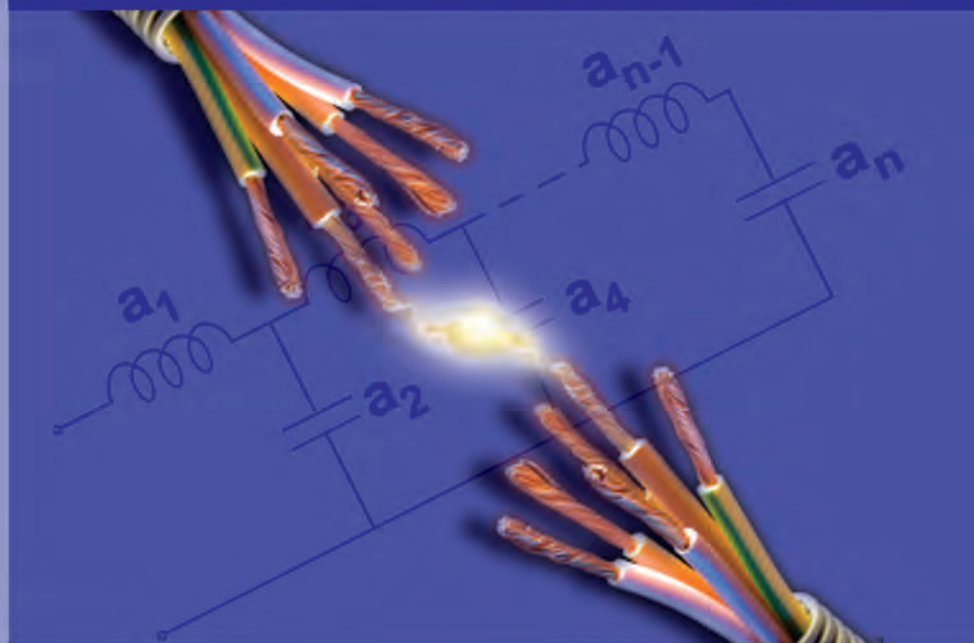


# Circuit Analysis

Second Edition

P. Ramesh Babu



SCITECH

*Knowledge for Ages*

ISBN: 9788183713535

# Circuit Analysis

**Second Edition**

**P. Ramesh Babu**

Pondicherry Engineering College,  
Pondicherry - 605 014.



Publishing for future

**SCITECH PUBLICATIONS (INDIA) PVT. LTD.**  
**CHENNAI**

## Contents

<b>Chapter 1</b>	<b>Basic Circuit Analysis</b>	<b>1.1 - 1.203</b>
1.1	Introduction . . . . .	1.1
1.2	Charge . . . . .	1.1
1.3	Conductors, Insulators and Semiconductors . . . . .	1.2
	1.3.1 Conductor . . . . .	1.2
	1.3.2 Insulator . . . . .	1.3
	1.3.3 Semiconductor . . . . .	1.3
1.4	Electric Current . . . . .	1.3
1.5	Coulomb's Law . . . . .	1.3
1.6	Electric Field . . . . .	1.4
	1.6.1 Electric field intensity . . . . .	1.5
	1.6.2 Electric flux density . . . . .	1.6
1.7	Voltage . . . . .	1.6
1.8	Work, Energy and Power . . . . .	1.10
1.9	Active and Passive Elements . . . . .	1.11
1.10	Independent Voltage Source . . . . .	1.11
1.11	Independent Current Source . . . . .	1.11
1.12	Series and Parallel Connected Sources . . . . .	1.12
	1.12.1 Series connected independent sources . . . . .	1.12
	1.12.2 Parallel connected independent sources . . . . .	1.12
1.13	Dependent Sources . . . . .	1.13
1.14	Resistance and Conductance . . . . .	1.14
	1.14.1 Resistance . . . . .	1.14
	1.14.2 Conductance . . . . .	1.14
1.15	Networks and Circuits . . . . .	1.14
1.16	Conventional Current . . . . .	1.15
1.17	Direct Current (dc) and Alternating Current (ac) . . . . .	1.16
1.18	Measuring Voltage and Current . . . . .	1.16
1.19	Ohm's Law . . . . .	1.17
1.20	Kirchhoff's Laws . . . . .	1.19

1.20.1	Kirchhoff's Current Law (KCL)	1.19
1.20.2	Kirchhoff's Voltage Law (KVL)	1.22
1.21	Single Loop Circuit	1.24
1.21.1	Resistors in series	1.25
1.22	Single Node-Pair Circuit	1.29
1.22.1	Resistors in parallel	1.30
1.23	Voltage Divider	1.33
1.24	Current Divider	1.34
1.25	Conductances in Parallel	1.38
1.26	Open Circuits	1.41
1.27	Short Circuits	1.43
1.28	Series - Parallel Circuits	1.46
1.29	Analysis of a Ladder Network	1.58
1.29.1	Analysis of R-2R ladder network	1.60
1.30	Equivalent Resistance	1.68
1.31	Nodal Analysis	1.73
1.31.1	Circuits containing voltage sources (supernode)	1.80
1.32	Mesh Analysis	1.85
1.32.1	Supermesh	1.91
1.33	Linearity, Proportionality and Superposition	1.110
1.33.1	Superposition theorem	1.112
1.34	Source Transformation	1.121
1.35	Thevenin's Theorem	1.124
1.36	Norton's Theorem	1.131
1.37	Maximum Power Transfer Theorem	1.143
1.38	Delta - Wye Transformations	1.148
1.39	Additional Theorems	1.154
1.39.1	Compensation theorem	1.154
1.39.2	Reciprocity theorem	1.157
1.40	Millman's Theorem	1.160
1.40.1	Capacitor	1.167
1.40.2	Inductor	1.178
1.40.3	Response of energy storage elements to DC sources	1.185



3.5	The Complex Forcing Function . . . . .	3.14
3.6	Complex Algebra . . . . .	3.15
	3.6.1 Polar form . . . . .	3.16
	3.6.2 Arithmetic operations . . . . .	3.16
3.7	Complex Plane . . . . .	3.24
3.8	The Operator $j$ . . . . .	3.24
3.9	Phasor Relationship for R, L and C . . . . .	3.26
	3.9.1 Resistor . . . . .	3.26
	3.9.2 Inductor . . . . .	3.27
	3.9.3 Capacitor . . . . .	3.28
3.10	Impedance . . . . .	3.28
3.11	Impedance Diagram . . . . .	3.30
3.12	Admittance . . . . .	3.30
3.13	Phasor Diagram . . . . .	3.33
	3.13.1 RL series circuit . . . . .	3.34
	3.13.2 RC series circuit . . . . .	3.35
	3.13.3 RLC series circuit . . . . .	3.37
3.14	Impedances in Series . . . . .	3.38
3.15	Impedances in Parallel . . . . .	3.39
3.16	AC Circuit Analysis . . . . .	3.39
3.17	Instantaneous Power . . . . .	3.55
3.18	Average Power . . . . .	3.56
3.19	RMS Value of Current and Voltage . . . . .	3.56
3.20	Apparent Power (Complex Power) and Power Factor . . . . .	3.57
3.21	Power Triangle . . . . .	3.59
3.22	AC Mesh Analysis . . . . .	3.63
3.23	AC Node Analysis . . . . .	3.64
3.24	Delta -Wye Transformations . . . . .	3.76
3.25	Source Transformation . . . . .	3.79
3.26	Superposition Theorem . . . . .	3.83
3.27	Thevenin's Theorem . . . . .	3.87
3.28	Norton's Theorem . . . . .	3.87
3.29	Maximum Power Transfer Theorem . . . . .	3.97
3.30	Reciprocity Theorem . . . . .	3.104







7.8.1	Overdamped response . . . . .	7.47
7.8.2	Underdamped response . . . . .	7.47
7.8.3	Critically damped response . . . . .	7.49
7.9	Parallel RLC Circuit . . . . .	7.49
7.10	Total Response of an RLC Series Circuit . . . . .	7.50
7.11	Laplace Transform . . . . .	7.73
7.12	Laplace Transform of Signal Waveforms . . . . .	7.74
7.12.1	Unit step function . . . . .	7.74
7.12.2	The shifted unit step function . . . . .	7.75
7.12.3	Unit ramp function . . . . .	7.75
7.12.4	Shifted ramp function . . . . .	7.76
7.12.5	Unit impulse function . . . . .	7.77
7.12.6	The exponential function . . . . .	7.77
7.13	Properties of Laplace Transform . . . . .	7.79
7.13.1	Linearity . . . . .	7.79
7.13.2	Transform of derivatives . . . . .	7.80
7.13.3	Transform of the integrals . . . . .	7.81
7.13.4	Scaling property . . . . .	7.82
7.13.5	Time shift . . . . .	7.82
7.13.6	Frequency shift . . . . .	7.83
7.13.7	Differentiation in the s - domain . . . . .	7.83
7.13.8	Time convolution . . . . .	7.84
7.13.9	Frequency convolution . . . . .	7.85
7.13.10	Initial value theorem . . . . .	7.85
7.13.11	Final value theorem . . . . .	7.86
7.14	Inversion of Laplace Transform . . . . .	7.96
7.14.1	Distinct roots . . . . .	7.97
7.14.2	Multiple roots . . . . .	7.98
7.14.3	Complex roots . . . . .	7.99
7.15	Solving Integrodifferential Equations . . . . .	7.103
7.16	Transient Analysis using Laplace Transforms . . . . .	7.106
7.17	Introduction to Complex Frequency . . . . .	7.137
7.18	Transform Impedance Elements . . . . .	7.139
7.18.1	Resistors in s - domain . . . . .	7.139

7.18.2	Inductor in s-domain . . . . .	7.139
7.18.3	Capacitor in s-domain . . . . .	7.140
7.19	Nodal and Mesh Analysis in s-domain . . . . .	7.143
7.20	Transfer Function . . . . .	7.148
7.21	Poles and Zeros of Transfer Function . . . . .	7.159
7.22	Complex Frequency Plane (s-plane) . . . . .	7.160
7.23	Convolution Integral . . . . .	7.162
7.24	Natural Response and s-plane . . . . .	7.168
	<i>Short Questions and Answers</i> . . . . .	7.170
	<i>Objective Type Questions</i> . . . . .	7.184

## **Chapter 8 Network Parameters and Network Functions 8.1 - 8.99**

8.1	Introduction . . . . .	8.1
8.2	Z-parameters . . . . .	8.1
8.3	Reciprocal Networks . . . . .	8.7
8.4	Y - Parameters . . . . .	8.9
8.5	Hybrid Parameters . . . . .	8.15
8.6	Transmission Parameters . . . . .	8.21
8.7	Inverse Transmission Parameters . . . . .	8.25
8.8	Relationships between Parameter Sets . . . . .	8.27
8.8.1	Y-parameters in terms of Z-parameters . . . . .	8.27
8.8.2	Z-parameters in terms of Y-parameters . . . . .	8.28
8.8.3	Z-parameters in terms of h-parameters . . . . .	8.29
8.8.4	h-parameters in terms of Z-parameters . . . . .	8.30
8.8.5	Y-parameters in terms of h-parameters . . . . .	8.30
8.8.6	h-parameters in terms of Y-parameters . . . . .	8.31
8.8.7	Z-parameters in terms of ABCD parameters . . . . .	8.31
8.8.8	ABCD parameters in terms of Z-parameters . . . . .	8.32
8.8.9	ABCD parameters in terms of h-parameters . . . . .	8.33
8.8.10	h-parameters in terms of ABCD parameters . . . . .	8.34
8.9	Transmission Parameters for Reciprocal Networks . . . . .	8.34
8.10	Two-Port Parameters in s-domain . . . . .	8.37
8.11	Cascade Connection of Two Two-Port Networks . . . . .	8.42
8.12	Parallel Connection of Two Two-Port Networks . . . . .	8.43
8.13	Series Connection of Two Two-Port Networks . . . . .	8.44

8.14 Series - Parallel Connection of Two Two-Port Networks . . . . .	8.45
8.15 Two-Port Network with Terminated Impedance . . . . .	8.57
8.16 Network Functions for Two-Port Network . . . . .	8.70
8.17 Poles and Zeros of Network functions . . . . .	8.83
<i>Short Questions and Answers</i> . . . . .	8.88
<i>Objective Type Questions</i> . . . . .	8.90

<b>Chapter 9</b>	<b>Fourier Series Analysis</b>	<b>9.1 - 9.47</b>
9.1	Introduction . . . . .	9.1
9.2	Periodic Waveforms . . . . .	9.1
9.3	Fourier Series . . . . .	9.2
9.4	Evaluation of Fourier Coefficients . . . . .	9.3
9.5	Even and Odd Symmetry . . . . .	9.9
9.6	Half Wave Symmetry . . . . .	9.12
9.7	Cosine Representation . . . . .	9.12
9.8	Exponential Fourier Series . . . . .	9.17
9.9	Existence of Fourier Series . . . . .	9.19
9.10	Properties of Fourier Series . . . . .	9.22
	9.10.1 Linearity . . . . .	9.22
	9.10.2 Time shifting . . . . .	9.23
	9.10.3 Time reversal . . . . .	9.23
	9.10.4 Time scaling . . . . .	9.23
	9.10.5 Multiplication . . . . .	9.23
	9.10.6 Conjugation . . . . .	9.23
	9.10.7 Parseval's theorem . . . . .	9.24
9.11	Power Representation using the Fourier Series . . . . .	9.25
9.12	Network Analysis using Fourier Series . . . . .	9.27
9.13	The Fourier Transform . . . . .	9.31
9.14	Existence of Fourier Transform . . . . .	9.33
9.15	Properties of Fourier Transform . . . . .	9.36
9.16	The Fourier Transform of General Periodic Time Functions . . . . .	9.40
9.17	The System Function and Response in the Frequency Domain . . . . .	9.41
9.18	Circuit Analysis with Fourier Transform . . . . .	9.42

<b>Chapter 10</b>	<b>Filters</b>	<b>10.1 - 10.77</b>
10.1	Introduction . . . . .	10.1
10.2	Frequency Selective Filters . . . . .	10.3
10.3	Lowpass filters . . . . .	10.4
10.3.1	The series RL circuit . . . . .	10.4
10.3.2	A series RC circuit . . . . .	10.6
10.4	Highpass Filter . . . . .	10.7
10.5	Bandpass Filters . . . . .	10.8
10.6	Bandreject Filters . . . . .	10.10
10.7	Second Order Lowpass Filter . . . . .	10.12
10.8	Second Order Highpass filter . . . . .	10.15
10.9	Ladder Networks . . . . .	10.24
10.9.1	Lowpass networks . . . . .	10.24
10.9.2	Highpass networks . . . . .	10.24
10.10	Lowpass Filter Section . . . . .	10.25
10.10.1	Nominal impedance . . . . .	10.27
10.11	'Constant-k' Prototype Lowpass Filter . . . . .	10.30
10.12	High-pass Filter Section . . . . .	10.35
10.12.1	Nominal impedance . . . . .	10.37
10.13	Constant K Prototype Highpass Filter . . . . .	10.39
10.14	m-derived Filter Section . . . . .	10.42
10.15	m-derived T-section . . . . .	10.43
10.16	m-derived $\pi$ -Section . . . . .	10.44
10.17	m-derived Lowpass Filter . . . . .	10.45
10.18	m-derived Highpass Filter . . . . .	10.49
10.19	Bandpass Filter . . . . .	10.51
10.20	Band Elimination Filter . . . . .	10.53
10.21	Analog Lowpass Filter Design . . . . .	10.58
10.21.1	Analog lowpass butterworth filter . . . . .	10.59
10.21.2	Analog lowpass chebyshev filters . . . . .	10.65
10.22	Frequency Transformation in Analog Domain . . . . .	10.72
10.22.1	Lowpass to lowpass . . . . .	10.72
10.22.2	Lowpass to highpass . . . . .	10.72

10.22.3 Lowpass to bandpass . . . . .	10.73
10.22.4 Lowpass to bandstop . . . . .	10.73

<b>Chapter 11</b>	<b>Attenuators</b>	<b>11.1 - 11.18</b>
-------------------	--------------------	---------------------

11.1 Introduction . . . . .	11.1
11.2 Symmetrical Network . . . . .	11.1
11.3 Characteristic Impedance . . . . .	11.1
11.4 Logarithmic Ratios . . . . .	11.4
11.5 Symmetrical T- Attenuator . . . . .	11.5
11.6 Symmetrical - II Attenuator . . . . .	11.8
11.7 Lattice Attenuator . . . . .	11.11
11.8 Bridged-T Attenuator . . . . .	11.13
11.9 Propagation Constant of Symmetrical Networks . . . . .	11.15
11.9.1 Symmetrical T- net work . . . . .	11.16
11.9.2 Symmetrical - II network . . . . .	11.17

<b>Chapter 12</b>	<b>Network Synthesis</b>	<b>12.1 - 12.28</b>
-------------------	--------------------------	---------------------

12.1 Introduction . . . . .	12.1
12.2 Hurwitz Polynomial . . . . .	12.2
12.3 Positive Real Function . . . . .	12.2
12.4 Synthesis of Driving Point Immittances . . . . .	12.9
12.4.1 Foster form I . . . . .	12.9
12.4.2 Foster form II . . . . .	12.10
12.4.3 Cauer form I . . . . .	12.11
12.4.4 Cauer form II . . . . .	12.11
<i>Short Questions and Answers</i> . . . . .	12.27

<b>Index</b>	<b>I.1 - I.4</b>
--------------	------------------

<b>References</b>	<b>R.1 - R.2</b>
-------------------	------------------

# Circuit Analysis

Second Edition

This textbook Circuit Analysis contains about 12 Chapters. It begins with the fundamentals of circuit analysis to attenuators and network synthesis are covered in detail. All topics in this text are explained in simple English. More than 650 problems are solved and around 200 objective type questions are given with solutions.

**Dr. P. Ramesh Babu** is currently working as Associate Professor in Pondicherry Engineering College Pondicherry - 605 014. He graduated in electronics and communication engineering from NBKR Institute of Science and Technology, S.V. University, Tirupati. He obtained his Ph.D from Indian Institute Technology Madras (IIT-M), Chennai. He is in teaching profession for more than 17 years. He is a life member of ISTE. His main areas of interest include Multivariate data analysis, Digital Signal Processing, Control Systems and Microprocessor based system design.



Publishing  
for  
future

**SCITECH PUBLICATIONS (INDIA) PVT. LTD.**

[www.scitechpublications.com](http://www.scitechpublications.com)

email: [scitechcorp@yahoo.co.in](mailto:scitechcorp@yahoo.co.in)

