

ISBN: 9788183715263

Linear Integrated Circuits and Applications

(As per latest AU Syllabus Code: EE6303)

T. R. Ganesh Babu

Associate Professor,

Department of Electronics and Communication Engineering,
Shri Andal Alagar College of Engineering,
Mamandur, Chennai.



Publishing for future

SCITECH PUBLICATIONS (INDIA) PVT. LTD.

www.scitechpublications.com

www.scitechpublications.com

Contents

Chapter 1	IC Fabrication	1 - 44
1.1	Introduction to Mass Technology	1
1.2	Classification of ICs	2
1.2.1	Based on complexity level	2
1.2.2	Based on the fabrication process	4
1.2.3	Based on the functions performed	4
1.3	Fundamentals of Monolithic IC Technology	4
1.4	Planner Processes	11
1.4.1	Silicon wafer fabrication	11
1.4.2	Epitaxial growth	13
1.4.3	Photolithography [Making and Etching]	14
1.4.4	Etching	15
1.4.5	Diffusion	16
1.4.6	Ion implantation	17
1.4.7	Oxidation	18
1.4.8	Metallization	19
1.4.9	Realization of monolithic ICs and packages	20
1.5	Construction of Bipolar Transistor	23
1.5.1	Planar-diffusion method	23
1.5.2	Epitaxial Method	25
1.6	Monolithic Diodes	27
1.7	Integrated Resistors	29
1.7.1	Diffused resistors	29
1.7.2	Epitaxial resistors	30
1.7.3	Ion implanted resistors	30
1.7.4	Pinch resistors	31
1.8	Integrated Circuit Capacitors	31
1.8.1	Diffused junction capacitor	31
1.8.2	MOS capacitor	32

1.9	Fabrication of FETs	33
1.9.1	Introduction to MOS process	34
1.9.2	Fabrication of nMOS transistor	35
	<i>Short Questions and Answers</i>	36
	<i>Review Questions</i>	43
Chapter 2	Characteristics of OP-amp	45 - 164
2.1	Introduction	45
2.2	Op-amp Symbols and Terminals	46
2.3	Block Diagram Representation of Op-amp	47
2.3.1	Input stage	48
2.3.2	Intermediate stage	48
2.3.3	Level shifter stage	49
2.3.4	Output stage	49
2.4	Input Stage of Op-amp	49
2.5	DC Level Shifting Stage	51
2.6	Output Stage in Op-Amp	54
2.7	Ideal Op-amp Characteristics	56
2.8	Equivalent Circuit of Op-Amp	58
2.9	DC Characteristics (Practical Op-amp Characteristics)	59
2.9.1	Input resistance	59
2.9.2	Output resistance	59
2.9.3	Input bias current	59
2.9.4	Input offset current	61
2.9.5	Input offset voltage	63
2.9.6	Total output offset voltage	64
2.9.7	Thermal Drift	65
2.10	AC Characteristics	67
2.10.1	Frequency response of operational amplifier	67
2.10.2	Stability of an op-amp	71
2.10.3	Frequency compensation	75
2.10.4	Slew rate	83

2.11	Power Supply Rejection Ratio	86
2.12	Transistorized Differential Amplifier	93
2.13	Analysis of Dual Input and Balanced Output Differential Amplifier	95
2.14	Configuration of Differential Amplifiers	105
2.15	Inverting Amplifier	109
2.16	Non-Inverting Amplifier	110
2.17	Voltage Follower	114
2.18	Voltage to Current Converter	115
2.18.1	Voltage to current converter with floating load	115
2.18.2	Voltage to current converter with grounded load	116
2.19	Current to Voltage Converter	117
2.20	Summing Amplifier	118
2.20.1	Inverting summing amplifier	118
2.20.2	Non-inverting summing amplifier	119
2.21	Subtractor or Difference Amplifier	120
2.22	Differential Amplifier with One Op-Amp	123
2.23	Integrator	129
2.23.1	Ideal active op-amp integrator	129
2.23.2	Non-inverting integrator	130
2.23.3	Practical integrator	131
2.23.4	Summing integrator	135
2.24	Differentiator	136
2.24.1	Ideal active op-amp differentiator	136
2.24.2	Practical differentiator	137
2.24.3	Summing differentiator	147
	Short Questions and Answers	157
	Review Questions	163

Chapter 3 Applications of Operational Amplifiers 165 - 302

3.1	Introduction	165
3.2	Instrumentation Amplifiers	165

3.3	Log and Antilog Amplifiers	167
3.3.1	Introduction	167
3.3.2	Log amplifier	167
3.3.3	Temperature compensated log amplifier	169
3.4	Antilog Amplifier	173
3.4.1	Basic antilog amplifier	173
3.4.2	Antilog amplifier using transistor	174
3.4.3	Temperature compensated antilog amplifier	177
3.5	Active Filters	179
3.5.1	Introduction	179
3.5.2	First order low pass filter	182
3.5.3	Second order active filter	185
3.5.4	Second order low pass filter	187
3.5.5	First order high pass filter	193
3.5.6	Second order high pass, Butterworth filter	195
3.5.7	Band pass filter	198
3.5.8	Wide band pass filter	204
3.5.9	Band stop filter	208
3.5.10	Notch filters	208
3.5.11	Wein-Bridge notch filter	210
3.6	Comparator	210
3.6.1	Introduction	210
3.6.2	Basic comparator (Non-inverting type)	211
3.6.3	Inverting comparator	212
3.6.4	Comparator characteristics	213
3.6.5	Application of comparator	214
3.7	Multivibrators	217
3.7.1	Introduction	217
3.7.2	Astable multivibrator	218
3.7.3	Monostable multivibrator	221
3.8	Waveform Generator	223
3.8.1	Triangular wave generator	224

3.9	Schmitt trigger	227
3.9.1	Regenerative comparator	227
3.9.2	Non-inverting schmitt trigger	229
3.10	Sinusoidal Oscillators	231
3.10.1	Introduction	231
3.10.2	Weinbridge oscillator	232
3.10.3	Colpitts oscillator	235
3.10.4	Hartley oscillator	236
3.10.5	RC phase shift oscillator	237
3.11	Clipper	241
3.12	Peak Detector	243
3.13	Ideal Clamper	244
3.14	Sample and Hold Circuits	247
3.15	D/A Converter	251
3.15.1	Introduction	251
3.15.2	Weighted resistor D/A converter	253
3.15.3	R-2R ladder D/A converter	257
3.16	Specifications for D/A Converters	263
3.17	A/D Converters	265
3.18	Direct Type ADCs	272
3.19	Successive Approximation A/D Converter	274
3.20	Single-Ramp (Single slope) ADC	276
3.21	Dual Slope A/D converter	279
3.22	A/D Converter using Voltage-to-Frequency Conversion	282
3.23	A/D Converter using Voltage-to-Time Conversion	284
3.24	Specifications for ADC	285
3.25	Source of Errors in ADC	286
	Short Questions and Answers	291
	Review Questions	300

Chapter 4	Special ICs	303 - 378
4.1	Introduction	303
4.2	Basics of IC 555 Timer	303
4.3	Monostable Multivibrator	307
4.4	Application of Monostable Multivibrator	310
4.4.1	Pulse width modulation	310
4.4.2	Pulse stretcher	311
4.4.3	Water level fill control	311
4.5	Astable Multivibrator	314
4.6	Application of Astable Multivibrator	318
4.6.1	Square wave oscillator	318
4.6.2	Free-running ramp generator	319
4.6.3	FSK generator	320
4.6.4	Pulse position modulator	321
4.7	Timer as Schmitt Trigger	326
4.8	Voltage Controlled Oscillator [VCO]	326
4.8.1	Voltage to frequency conversion factor	329
4.8.2	Features of 566 VCO	329
4.8.3	Applications of VCO	330
4.9	Phase-Locked Loop	330
4.9.1	Introduction	330
4.9.2	Lock and capture range	331
4.9.3	Voltage-Controlled Oscillator	333
4.10	Phase Detector/ Comparator	333
4.10.1	Analog phase detector	334
4.10.2	Balanced modulator type phase detector	335
4.11	Digital Phase Detector	338
4.11.1	X-OR phase detector	338
4.11.2	Flip-flop phase detectors	339
4.11.3	Phase-frequency detector	340
4.12	Monolithic Phase Locked Loops	341

4.13 Derivation of Lock-in-Range and Capture Range	344
4.13.1 Lock-in-range	344
4.13.2 Capture range	345
4.14 Transfer Characteristics of PLL	348
4.15 565 PLL Applications	349
4.15.1 Frequency multiplier	349
4.15.2 Frequency Shift Keying (FSK) demodulator	351
4.15.3 Frequency translation	354
4.15.4 PLL as frequency synthesizer	355
4.15.5 AM detection	356
4.15.6 FM detector	356
4.16 Analog Voltage Multiplier Circuit	357
4.17 Analog Voltage Divider Circuit	358
4.18 Multipliers	359
4.18.1 Multiplier IC	359
4.18.2 Multiplier characteristics	361
4.19 Application of Multiplier	363
4.19.1 Voltage divider using multiplier	364
4.19.2 Squaring circuit using multiplier	364
4.19.3 Square rooting circuit using multiplier	365
4.19.4 Frequency doubler using multiplier	366
4.19.5 Phase angle detection using multiplier	368
4.19.6 RMS detector [Root Mean Square]	369
4.19.7 Multipliers used as rectifier	369
4.20 Multiplier IC AD 533	370
4.20.1 Pin diagram of AD 533	370
4.20.2 AD 533 as a multiplier	371
Short Questions and Answers	372
Review Questions	377

Chapter 5	Application ICs	379 - 424
5.1	Introduction	379
5.2	IC Voltage Regulator	380
5.2.1	Introduction	380
5.2.2	Performance parameters	381
5.2.3	Characteristics of voltage regulators	383
5.2.4	Basic op-amp series regulator	384
5.2.5	Basic op-amp shunt regulator	385
5.2.6	Fixed voltage regulator	386
5.2.7	The positive voltage regulator used as a current source	387
5.2.8	Current booster	387
5.2.9	Negative voltage regulator	388
5.2.10	Adjustable voltage regulator	389
5.2.11	Dual power supply	391
5.3	General Purpose Regulator	393
5.3.1	Introduction	393
5.3.2	723 voltage regulator - Important features	394
5.3.3	Electrical characteristics	394
5.4	Internal Structure of IC 723	396
5.5	Application of IC 723	397
5.5.1	Basic Low-voltage regulator [$V_0 = 2$ to 7 Volts]	397
5.5.2	High voltage 723 regulator	398
5.5.3	Current boosting	399
5.6	Switched Regulator	399
5.6.1	Switching regulator or Switched Mode Power Supply (SMPS)	399
5.7	Types of Switching Regulator	402
5.7.1	Step down switching regulator(BUCK - converter)	402
5.7.2	Step up switching regulator (BOOST - converter)	403
5.7.3	Inverting switching regulator (BUCK BOOST - converter)	404
5.7.4	IC switched regulator	405

5.8	Power Amplifier	408
5.8.1	Introduction	408
5.8.2	LM 380 power audio amplifier	408
5.8.3	Application of LM380 audio power amplifier	410
5.9	Function Generator	417
	<i>Short Questions and Answers</i>	420
	<i>Review Questions</i>	423
	Index	425 - 428
	References	429

