

Linear Integrated Circuits

Sixth Edition

Dr. T. R. Ganesh Babu

Professor,

Department of Electronics and Communication Engineering,
Muthayammal Engineering College,
Rasipuram, Namakkal (Dt) - 637 408.

B. Suseela

Former Associate Professor

Department of Electronics and Communication Engineering,
Roever Engineering College,
Elambalur,
Perambalur (Dt) - 621 212.



Publishing for future

SCITECH PUBLICATIONS (INDIA) PVT. LTD.

www.scitechpublications.com

Contents

Chapter 1	Basics of Operational Amplifiers	1.1 - 1.123
1.1	Introduction	1.1
1.2	Fundamentals of Differential Amplifier	1.1
1.3	Transistorized Differential Amplifier	1.8
1.4	Analysis of Dual Input and Balanced Output Differential Amplifier	1.10
1.5	Configuration of Differential Amplifiers	1.21
1.6	Methods for Improving CMRR	1.25
1.7	Current Sources	1.26
1.7.1	Differential amplifier with current source	1.26
1.7.2	Temperature compensation	1.28
1.7.3	Current source bias using zener diode	1.29
1.7.4	Current source used an active loads	1.30
1.8	Voltage Source	1.31
1.8.1	Impedance transformation	1.31
1.8.2	Use the negative feedback to reduce the output impedance	1.33
1.9	Voltage References	1.34
1.9.1	Voltage reference circuit using temperature compensation	1.35
1.9.2	Voltage reference using avalanche diode reference	1.37
1.9.3	Bandgap reference circuit	1.38
1.10	Current Mirrors	1.41
1.10.1	Circuit analysis	1.42
1.10.2	Improved current mirror circuit with beta helper	1.44
1.10.3	Wilson current source circuit	1.45
1.10.4	Widlar current source	1.48
1.10.5	Current mirror with magnification	1.52
1.10.6	Multiple current source	1.53
1.11	Differential Voltage Gain Improvement using Active Load	1.57
1.12	Op-amp Symbols and Terminals	1.59
1.13	Block Diagram Representation of Op-Amp	1.61

1.13.1	Input stage	1.61
1.13.2	Intermediate stage	1.62
1.13.3	Level shifter stage	1.62
1.13.4	Output stage	1.63
1.14	Input Stage of Op-Amp	1.63
1.15	DC Level Shifting Stage	1.65
1.16	Output Stage in Op-Amp	1.68
1.17	Ideal Op-Amp	1.70
1.18	Equivalent Circuit of Op-Amp	1.72
1.19	Practical Op-Amp Characteristics [DC Characteristics]	1.73
1.19.1	Input resistance	1.73
1.19.2	Output resistance	1.73
1.19.3	Input bias current	1.73
1.19.4	Input offset current	1.75
1.19.5	Input offset voltage	1.77
1.19.6	Total output offset voltage	1.78
1.19.7	Thermal drift	1.79
1.20	Open Loop Configuration Op-Amp	1.81
1.20.1	Differential amplifier	1.81
1.20.2	Inverting amplifier	1.82
1.20.3	Non inverting amplifier	1.83
1.21	Closed Loop Operation of Op-Amp	1.84
1.22	Realistic Simplifying Assumptions	1.84
1.22.1	Zero input current	1.84
1.22.2	Virtual ground	1.85
1.23	AC Characteristics	1.86
1.23.1	Frequency response	1.86
1.23.2	Stability of an op-amp	1.90
1.23.3	Frequency compensation	1.94
1.23.4	Slew rate	1.102
1.24	Power Supply Rejection Ratio	1.105
1.25	Op-Amp Packages	1.112

<i>Questions with Short Answers</i>	1.114
<i>Review Questions</i>	1.122

Chapter 2	Applications of Operational Amplifiers	2.1 - 2.125
2.1	Introduction	2.1
2.2	Inverting Amplifier	2.2
2.3	Non-Inverting Amplifier	2.3
2.4	Phase Shift Circuit	2.7
2.5	Voltage Follower	2.9
2.6	Voltage to Current Converter	2.9
2.6.1	Voltage-to-current converter with floating load	2.9
2.6.2	Voltage-to-current converter with grounded load	2.10
2.7	Current to voltage converter	2.12
2.7.1	Current to voltage converter	2.12
2.8	Summing Amplifier	2.13
2.8.1	Inverting summing amplifier	2.13
2.8.2	Non-inverting summing amplifier	2.14
2.9	Application of Summing Amplifier	2.15
2.9.1	Averaging amplifier	2.15
2.9.2	Subtractor or difference amplifier	2.16
2.10	Scaling or Weighted Amplifier	2.17
2.11	Differential Amplifier with One Op-Amp	2.20
2.12	Instrumentation Amplifiers	2.25
2.13	Integrator	2.27
2.13.1	Ideal active op-amp integrator	2.27
2.13.2	Non-inverting integrator	2.29
2.13.3	Practical integrator	2.30
2.13.4	Summing integrator	2.34
2.14	Differentiator	2.35
2.14.1	Ideal active op-amp differentiator	2.35
2.14.2	Practical differentiator	2.37
2.14.3	Summing differentiator	2.41

2.15	Log and Antilog Amplifiers	2.42
2.15.1	Introduction	2.42
2.15.2	Log amplifier	2.43
2.15.3	Temperature compensated log amplifier	2.44
2.16	Antilog Amplifier	2.49
2.16.1	Basic antilog amplifier	2.49
2.16.2	Antilog amplifier using transistor	2.50
2.16.3	Temperature compensated antilog amplifier	2.53
2.17	Comparator	2.55
2.17.1	Introduction	2.55
2.17.2	Basic comparator (Non-inverting type)	2.55
2.17.3	Inverting comparator	2.56
2.17.4	Comparator characteristics	2.57
2.17.5	Application of comparator	2.58
2.18	Schmitt Trigger	2.61
2.18.1	Regenerative comparator	2.61
2.18.2	Non-inverting schmitt trigger	2.63
2.19	Precision Rectifiers	2.65
2.19.1	Introduction	2.65
2.19.2	Precision half wave rectifier	2.66
2.19.3	Full wave rectifier	2.67
2.19.4	Clipper	2.69
2.19.5	Peak detector	2.71
2.19.6	Ideal clamper	2.72
2.20	Active Filters	2.74
2.20.1	Introduction	2.74
2.20.2	First order low pass filter	2.77
2.20.3	Second order active filter	2.81
2.20.4	Second order low pass filter	2.83
2.20.5	First order high pass, Butterworth filter	2.88
2.20.6	Second order high pass, Butterworth filter	2.90
2.20.7	Band pass filter	2.93

4.3.3	R-2R ladder D/A converter	4.12
4.3.4	Inverted R-2R ladder DAC	4.18
4.3.5	Analog switches	4.20
4.3.6	Monolithic DAC	4.21
4.4	Digital to Analog Converter with Binary Weighted Current Source	4.24
4.5	Specifications for D/A Converters	4.25
4.6	Sources of Errors in DAC	4.28
4.7	A/D Converters	4.29
4.8	Direct type ADCs	4.35
4.9	Successive Approximation A/D Converter	4.37
4.10	Single-Ramp (Single slope) ADC	4.40
4.11	Dual Slope A/D converter	4.42
4.12	A/D Converter using Voltage-to-Frequency Conversion	4.45
4.13	A/D Converter using Voltage-to-Time Conversion	4.47
4.14	Over sampling A/D converter	4.49
4.15	Specifications for ADC	4.51
4.16	Source of Errors in ADC	4.52
	Questions with Short Answers	4.57
	Review Questions	4.63

Chapter 5 Waveform Generators and Special Function ICs

5.1 - 5.131

5.1	Introduction	5.1
5.2	Sinewave Oscillators	5.1
5.2.1	Introduction	5.1
5.2.2	Weinbridge oscillator	5.2
5.2.3	Colpitts oscillator	5.5
5.2.4	Hartley oscillator	5.6
5.2.5	RC phase shift oscillator	5.7
5.3	Multivibrators	5.11
5.3.1	Introduction	5.11
5.3.2	Astable multivibrator	5.12

5.3.3	Monostable multivibrator	5.15
5.4	Triangular Wave Generator	5.18
5.5	Saw Tooth Wave Generator	5.22
5.6	Function Generator	5.25
5.7	Basics of IC 555 Timer	5.28
5.8	Monostable Multivibrator	5.32
5.9	Application of Monostable Multivibrator	5.35
5.9.1	Pulse width modulation	5.35
5.9.2	Pulse stretcher	5.35
5.9.3	Water level fill control	5.36
5.10	Astable Multivibrator	5.39
5.11	Application of Astable Multivibrator	5.43
5.11.1	Square wave oscillator	5.43
5.11.2	Free-running ramp generator	5.44
5.11.3	FSK generator	5.45
5.11.4	Pulse position modulator	5.46
5.12	Timer as Schmitt Trigger	5.50
5.13	IC Voltage Regulator	5.51
5.13.1	Introduction	5.51
5.13.2	Performance parameters	5.53
5.13.3	Characteristics of voltage regulators	5.54
5.13.4	Basic op-amp series regulator	5.55
5.13.5	Basic op-amp short regulator	5.56
5.13.6	Fixed voltage regulator	5.57
5.13.7	The positive voltage regulator used as a current source	5.58
5.13.8	Current booster	5.59
5.13.9	Negative voltage regulator	5.59
5.13.10	Adjustable voltage regulator	5.60
5.13.11	Dual power supply	5.62
5.14	General Purpose Regulator	5.64
5.14.1	Introduction	5.64
5.14.2	723 voltage regulator - important features	5.65

5.14.3	Electrical characteristics	5.65
5.15	Internal Structure of IC 723	5.67
5.16	Application of IC 723	5.68
5.16.1	Basic low-voltage regulator [$V_0 = 2$ to 7 Volts]	5.68
5.16.2	High voltage 723 regulator	5.69
5.16.3	Current boosting	5.70
5.17	Switched Regulator	5.70
5.17.1	Switching regulator or Switched Mode Power Supply (SMPS)	5.70
5.18	Types of Switching Regulator	5.73
5.18.1	Step down switching regulator(BUCK - converter)	5.73
5.18.2	Step up switching regulator (BOOST - converter)	5.74
5.18.3	Inverting switching regulator (BUCK BOOST - converter)	5.75
5.18.4	IC switched regulator	5.76
5.19	Switched Capacitor Filter	5.77
5.20	Switched Capacitor Integrator	5.80
5.20.1	MOSFET realization of switched capacitor filter	5.82
5.20.2	Switched capacitor filter IC MF10	5.86
5.21	Voltage to Frequency Converter	5.88
5.21.1	Voltage to FC	5.88
5.21.2	Frequency to voltage converter	5.93
5.22	Tuned Amplifiers	5.97
5.22.1	Introduction	5.97
5.22.2	IC tuned amplifier	5.98
5.23	Power Amplifier	5.99
5.23.1	Introduction	5.99
5.23.2	LM 380 power audio amplifier	5.100
5.23.3	Application of LM380 audio power amplifier	5.103
5.24	Isolation Amplifier	5.109
5.25	Video Amplifiers	5.111
5.26	Fiber Optics	5.114
5.27	Opto-Coupler	5.117

Questions with Short Answers 5.122
Review Questions 5.129

Fully Solved University Question Papers

UQ.1-UQ.39

Index

I.1-I.4

References

