

ISBN: 9788183716116

# **SOLID STATE DRIVES**

**K. MALARVIZHI**

*Senior Lecturer*

Department of Electrical and Electronics Engineering  
Kumaraguru College of Technology  
Coimbatore

**SCITECH PUBLICATIONS (INDIA) PVT. LTD.**

**CHENNAI & HYDERABAD**

[www.scitechpublications.com](http://www.scitechpublications.com)

# Contents

<b>Chapter 1</b>	<b>Electric Drive Characteristics</b>	<b>1.1-1.59</b>
1.1	Introduction	1.1
1.1.1	Classification of Electric Drive	1.1
1.1.2	Block diagram of a simple electric drive	1.3
1.2	Selection of Electric Drives	1.4
1.2.1	Factors to be considered	1.4
1.3	Advantages of Electric Drive over Mechanical Drive	1.8
1.4	Speed-Torque Characteristics of an Electric Drive	1.8
1.4.1	Types of loads	1.8
1.5	Joint Speed-Torque Characteristics	1.9
1.5.1	Quadrantal diagram of speed-torque characteristics	1.9
1.5.2	Multiquadrant dynamics in the speed torque plane	1.10
1.6	Typical load torque characteristics	1.12
1.6.1	Classes of motor duty	1.13
1.6.2	Load Equalisation	1.17
1.7	Nature of speed, torque and applications of different types of electric drives - Summary	1.17
1.8	Power Semiconductor Controlled Drives - An Introduction	1.19
1.8.1	Function of a Power Modulator	1.19
1.8.2	Advantages of electrical drives	1.20
1.8.3	Requirements or choice of an Electrical Drive	1.20
1.9	Rating and Heating of Electric drives	1.20
1.9.1	Requirements	1.20
1.10	Power Losses and Heating of Electric Drives	1.21
1.10.1	Thermal model of an electric motor for heating and cooling	1.22
1.10.2	Cooling curve	1.26
1.11	Starting, and Braking of DC motors	1.32
1.11.1	Starting	1.32
1.11.2	Braking	1.33
1.11.3	Types of Braking	1.33
1.12	Drive Classification Based on Speed Control	1.37
1.12.1	Single speed drive (or) Constant speed drive	1.37
1.12.2	Multispeed drive (or) variable speed drive	1.37
1.12.3	One quadrant drive	1.38
1.12.4	Two Quadrant Drive	1.38
1.12.5	Four Quadrant Drive	1.38
1.13	Solved Problems	1.39
1.14	Comparison Between DC And AC Drives	1.46
1.15	Transfer Function of DC Motors	1.46

1.16	Constant Torque and Constant Power (hp) Operations of DC motors	1.49
1.16.1	Armature voltage control mode	1.49
1.16.2	Field control mode	1.51
1.17	Equations Governing Motor Load Dynamics	1.52
1.17.1	Components of load torque	1.53
1.18	Equilibrium Operating Point and Steady State Stability of An Electric Drive	1.53
1.18.1	Coefficient of adhesion	1.55
1.19	Short Questions and Answers	1.55
1.20	Review Questions	1.57
1.21	Unsolved Problems	1.58

## Chapter 2 DC Drives

2.1-2.95

2.1	Introduction	2.1
2.2	Fundamentals of Most Commonly used Power Semiconductor Devices	2.1
2.3	Converters	2.11
2.3.1	Performance Parameters of Diode Rectifiers	2.14
2.4	Layout of a DC drive	2.17
2.5	Single Phase Thyristor Phase-Controlled Converter Fed Drives	2.19
2.5.1	Half-wave controlled	2.19
2.5.2	Half controlled converter [Semi Converter]	2.19
2.5.3	Fully controlled	2.20
2.5.4	Dual converter	2.20
2.6	Single Phase Separately Excited DC Motor Drives	2.21
2.6.1	Half controlled converter fed DC motor drive (Semi converter) with continuous motor current operation	2.21
2.6.2	Fully controlled converter fed dc motor drive with continuous motor current operation	2.23
2.6.3	Half-controlled converter fed dc motor drive with discontinuous motor current operation	2.29
2.6.4	Fully-controlled converter fed dc motor drive with discontinuous motor current operation	2.31
2.6.5	Conclusion	2.32
2.6.6	Effect of armature circuit inductance ' $L_a$ '	2.34
2.7	Single-Phase Series dc Motor Drives	2.36
2.7.1	Half-controlled converter fed dc series motor drive	2.38
2.7.2	Fully controlled converter fed dc series motor	2.39
2.7.3	Speed-torque characteristics	2.40
2.8	Three Phase Drives	2.41
2.8.1	Three phase semi-converter controlled DC motor drive	2.41
2.8.2	Three phase full-converter controlled DC motor drive	2.44
2.9	Solved Problems	2.46

2.10	Dual Converter fed DC Motor Drive	2.56
2.10.1	Without circulating current	2.57
2.10.2	With circulating current	2.59
2.11	Solved Problems	2.61
2.12	Chopper Controlled DC Drives	2.66
2.12.1	Introduction	2.66
2.13	DC chopper	2.68
2.14	Control Techniques used in dc Choppers	2.72
2.14.1	Time ratio control [TRC]	2.72
2.14.2	Current Limit Control [CLC]	2.72
2.15	Chopper Control of Separately Excited DC Motors	2.73
2.15.1	Motoring control (or) class A chopper drive (or) step down chopper	2.73
2.15.2	Regenerative braking or Stepup chopper or class B chopper drive	2.76
2.15.3	Dynamic braking control	2.78
2.15.4	Forward motoring and forward regenerative braking control (or) Class C chopper drive	2.79
2.15.5	Forward motoring and reverse regeneration control or class D chopper drive	2.81
2.15.6	Class E chopper fed drive (or) Four quadrant operation of chopper	2.82
2.16	Solved Problems	2.84
2.17	Closed Loop Control Of Dc Drives	2.87
2.17.1	Operation Below Rated Speed	2.88
2.17.2	Operation Above Rated Speed	2.88
2.18	Solved Problems	2.89
2.19	Short Questions and Answers	2.91
2.20	Review Questions	2.93
2.21	Unsolved Problems	2.94

### **Chapter 3 Stator Controlled Induction Motor Drives 3.1-3.54**

3.1	Introduction	3.1
3.1.1	Fundamental principles of induction machines	3.2
3.1.2	Equivalent circuit of an induction motor	3.3
3.1.3	Speed-Torque characteristics	3.5
3.1.4	Torque-slip characteristics	3.6
3.1.5	Electrical braking of induction motor	3.7
3.1.6	Comparison between Mechanical Braking and Electrical Braking	3.8
3.2	Types of Electric Braking of an Induction Motor	3.9
3.2.1	Regenerative braking	3.9
3.2.2	Dynamic braking (or) rheostatic braking	3.11
3.2.3	Plugging (or) Reverse current braking	3.13

3.3	Solved Problems	3.15
3.4	Speed Control Methods in Power Semiconductor Controlled Induction Motor Drives	3.17
	3.4.1 Stator controlled induction motor drives	3.17
3.5	Constant torque and Constant Power Operation	3.20
	3.5.1 Speed-torque curves: [For adjustable frequency method]	3.22
	3.5.2 Voltage-frequency curve	3.23
3.6	Voltage/Frequency Control [V/f Control]	3.25
3.7	Control of Induction Motors by AC Voltage Controllers [Soft Start of Induction Motor]	3.27
	3.7.1 Variable voltage AC motor drives	3.27
	3.7.2 Three phase full wave AC voltage controller for star connected load	3.28
	3.7.3 For Delta-connected load	3.29
	3.7.4 Four-Quadrant Drive [Reversible Drive]	3.29
3.8	Closed Loop Control of IM Using Stator Voltage Controller	3.31
3.9	Variable Frequency AC Motor Drives	3.32
	3.9.1 Static frequency changers	3.32
3.10	Three Phase Inverters	3.35
3.11	Voltage Source Inverter fed Drives [VSI Fed Drives]	3.35
3.12	Speed Control Schemes for Induction Motor by Voltage Source Inverters	3.36
	3.12.1 VSI fed IM drive with dynamic braking	3.37
	3.12.2 VSI fed IM drive with regenerative Braking	3.38
3.13	Solved Problems	3.39
3.14	Current Source Inverter fed Drives [CSI fed drives]	3.41
3.15	Speed Control Schemes for Induction Motor by Current Source Inverters	3.41
	3.15.1 Chopper controlled scheme	3.43
	3.15.2 Closed loop control	3.44
	3.15.3 Speed torque characteristics [for CSI fed drive]	3.44
3.16	Solved Problems	3.46
3.17	Short Questions and Answers	3.50
3.18	Review Questions	3.52
3.19	Unsolved Problems	3.53

#### **Chapter 4 Rotor Controlled Induction Motor Drives 4.1-4.41**

4.1	Introduction	4.1
4.2	Control techniques used in rotor controlled induction motor drives	4.2
	4.2.1 Conventional rotor resistance control	4.2
	4.2.2 Static rotor resistance control [Electronic control]	4.3
4.3	Approximate Equivalent Circuit [Static Rotor Resistance Control] and Speed-Torque Characteristics	4.6
4.4	Closed Loop Control for Static Rotor Resistance Control	4.8

4.5	Solved Problems	4.9
4.6	Injection of Voltage in the rotor Circuit	4.15
4.6.1	Operation with a fixed $V_r$ of positive polarity and phase sequence	4.16
4.6.2	Operation with $V_r$ of reversed polarity and phase sequence	4.18
4.6.3	Operation with controlled magnitude and phase angle of injected voltage	4.20
4.7	Slip Power Recovery Scheme	4.20
4.7.1	Power flow diagram	4.20
4.7.2	Theoretical principles of slip energy recovery scheme	4.21
4.8	Scherbius System	4.23
4.8.1	Conventional scherbius system [Traditional scherbius system]	4.23
4.8.2	Static scherbius system (DC link type)	4.24
4.9	Kramer System	4.31
4.9.1	Conventional Kramer system	4.31
4.9.2	Static Kramer system	4.33
4.10	Closed-Loop Control Operation	4.34
4.11	Power Factor Improvement	4.35
4.12	Commutatorless Kramer Drive System	4.37
4.13	Short Questions and Answers	4.38
4.14	Review Questions	4.39
4.15	Unsolved Problems	4.40

## Chapter 5 Synchronous Motor Drives

5.1-5.41

5.1	Introduction	5.1
5.1.1	Types of Synchronous Motors	5.2
5.1.2	Operation of a wound-field cylindrical rotor motor	5.3
5.1.3	Motoring and regenerative braking operations	5.4
5.1.4	Pull-out Torque	5.7
5.1.5	Pull-in Process	5.8
5.1.6	Steady-state stability limit (Maximum load torque)	5.9
5.1.7	Dynamic stability	5.9
5.1.8	Dynamic braking	5.10
5.2	Speed Control of Synchronous Motors	5.11
5.2.1	True synchronous mode	5.11
5.2.2	Self-controlled mode	5.14
5.3	Variable frequency system Control of synchronous motor	5.17
5.3.1	Voltage Source Inverter (VSI) fed synchronous motor drives	5.17
5.3.2	Braking in VSI fed drive	5.19
5.3.3	Power factor of VSI fed SM drive	5.20
5.4	Current Source Inverter (CSI) Fed Synchronous Motor Drive	5.20
5.4.1	LCI self-controlled synchronous motor drive [CLM mode]	5.21

5.5	Controlled Current Operation	5.24
5.6	Effect of Load Angle	5.25
5.7	Line Commutated Cycloconverter fed Synchronous Motor Drive	5.27
5.8	Closed Loop Control of Wound-Field Synchronous Motor Drive	5.28
	5.8.1 Motor Power Factor Control	5.28
5.9	Brushless Excitation	5.30
5.10	Solved Problems	5.31
5.11	Short Questions and Answers	5.38
5.12	Review Questions	5.39
5.13	Unsolved Problems	5.40
	Bibliography	